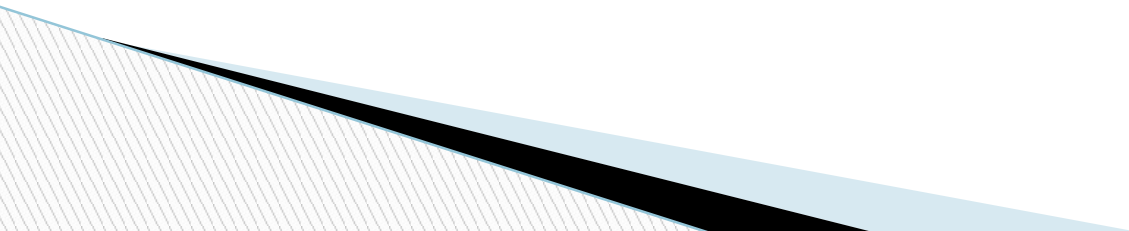


INTRODUCTION TO STICK DIAGRAMS AND LAYOUTS



STICK DIAGRAMS

▣ Objectives:


- To know what is meant by stick diagram.
- To understand the capabilities and limitations of stick diagram.
- To learn how to draw stick diagrams for a given MOS circuit.

▣ Outcome:

- At the end of this module the students will be able draw the stick diagram for simple MOS circuits.

Definition

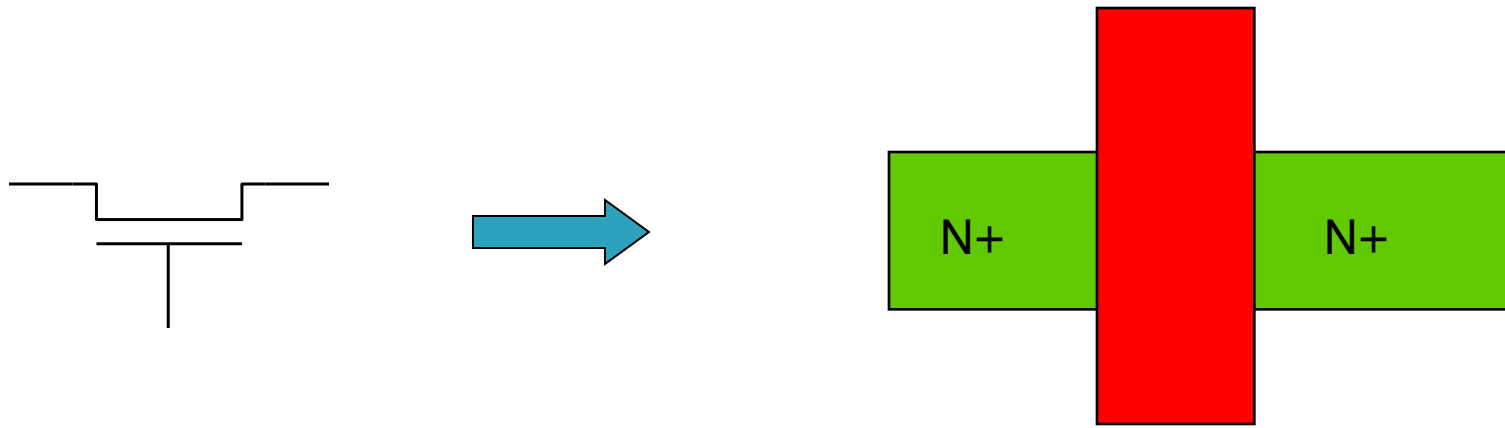Stick diagrams convey layer information through colour codes (or monochrome encoding). Acts as an interface between symbolic circuit and the actual layout.





When n-diffusion(green) crosses with poly(red) creates nMOS

When p-diffusion crosses with poly creates pMOS


Stick diagram of an CMOS

Inverter Stick

Circuit
diagram

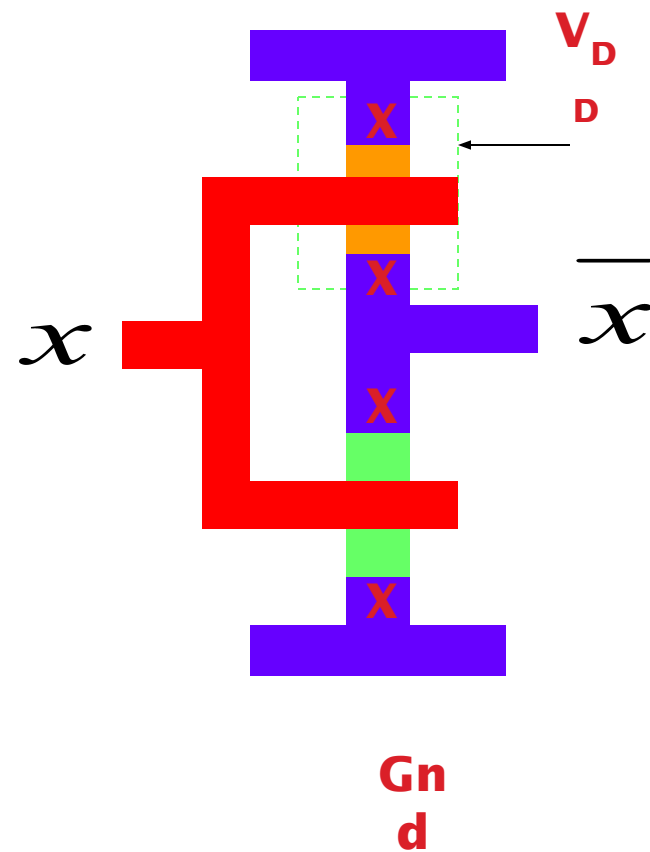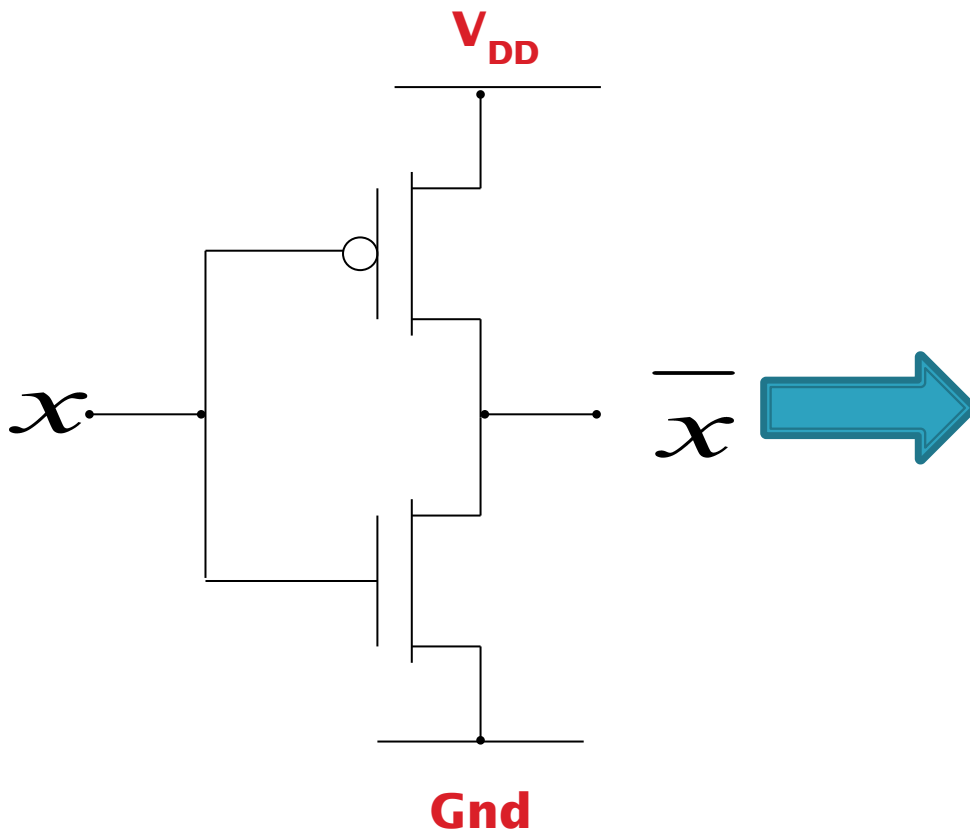

Stick diagram

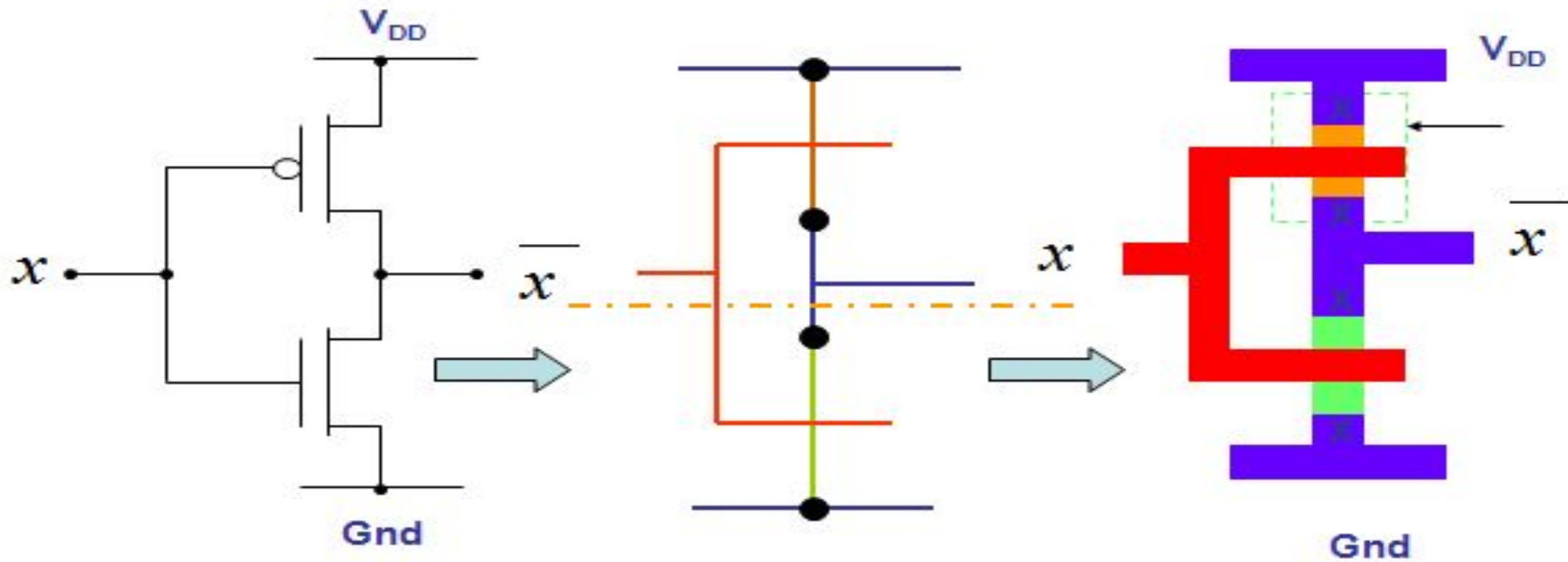

Blue = Metal 1

Orange = p- diffusion

Green = n-diffusion

Red = polysilicon

Stick Diagrams – Notations


Metal 1



poly



ndiff

 

pdiff



Can also draw
in shades of
gray/line style.

Stick Diagrams - Some Rules to follow

Rule 1.

When two or more 'sticks' of the same type cross or touch each other that represents electrical contact.



Rule 2.

When two or more 'sticks' of different type cross or touch each other there is no electrical contact.
(If electrical contact is needed we have to show the connection explicitly).



Rule 3.

When a poly crosses diffusion it represents a transistor.



Rule 4.



In CMOS a demarcation line is drawn to avoid touching of p-diff with n-diff. All pMOS must lie on one side of the line and all nMOS will have to be on the other side.



Note: If a contact is shown then it is **not** a creation of transistor.

2-input NAND gate



TWO INPUT NAND GATE

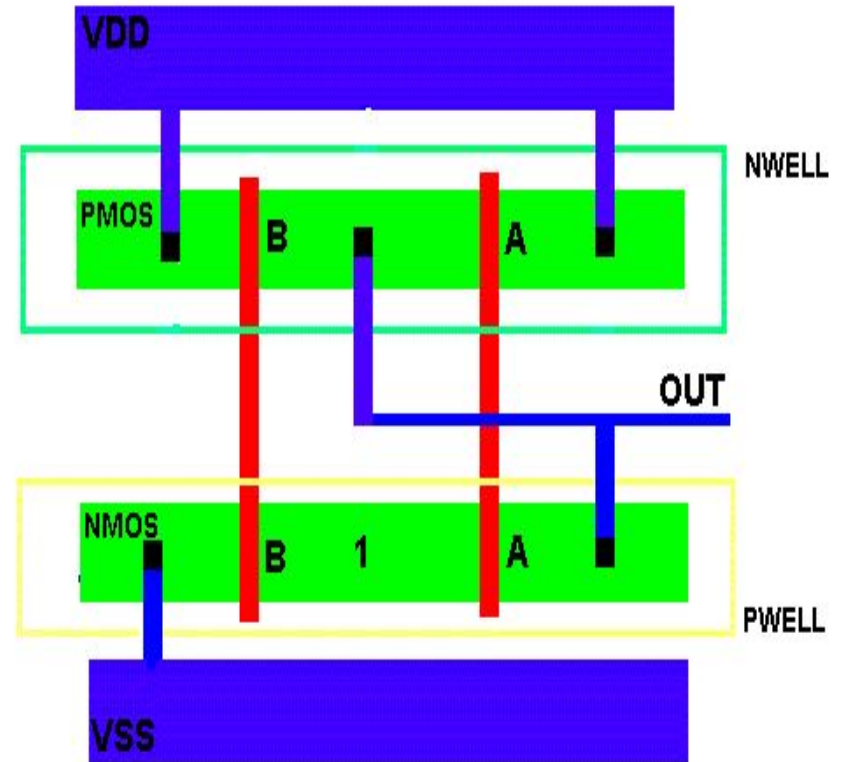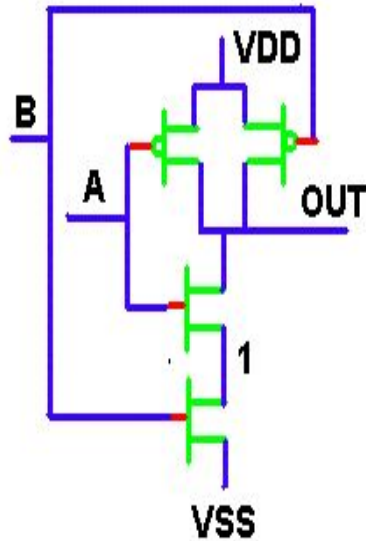



<u>MINIMUM SIZE GATE</u>	<u>SIZED GATES</u>	
	NMOS	PMOS
LENGTH = 2	$\frac{W}{L} \frac{8}{2}$	$\frac{W}{L} \frac{12}{2}$
WIDTH = 4		

- POLY
- METAL 1
- ACTIVE



Two inputs nMOS NAND Gate

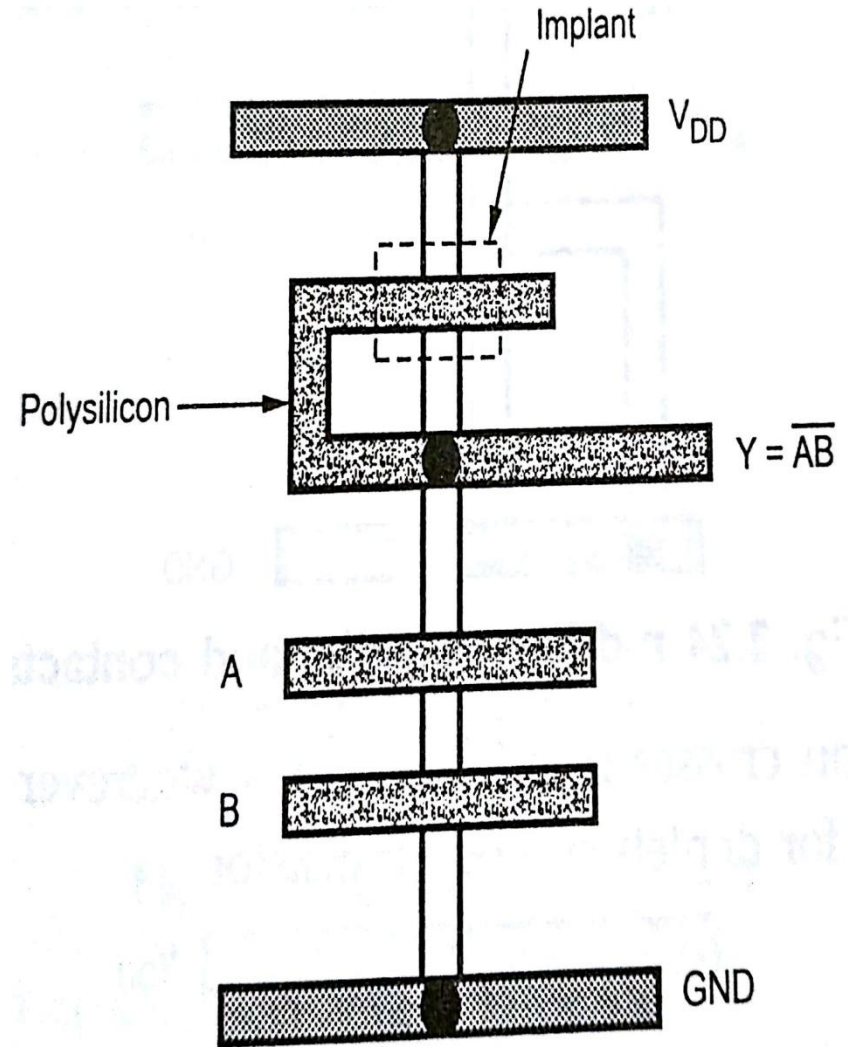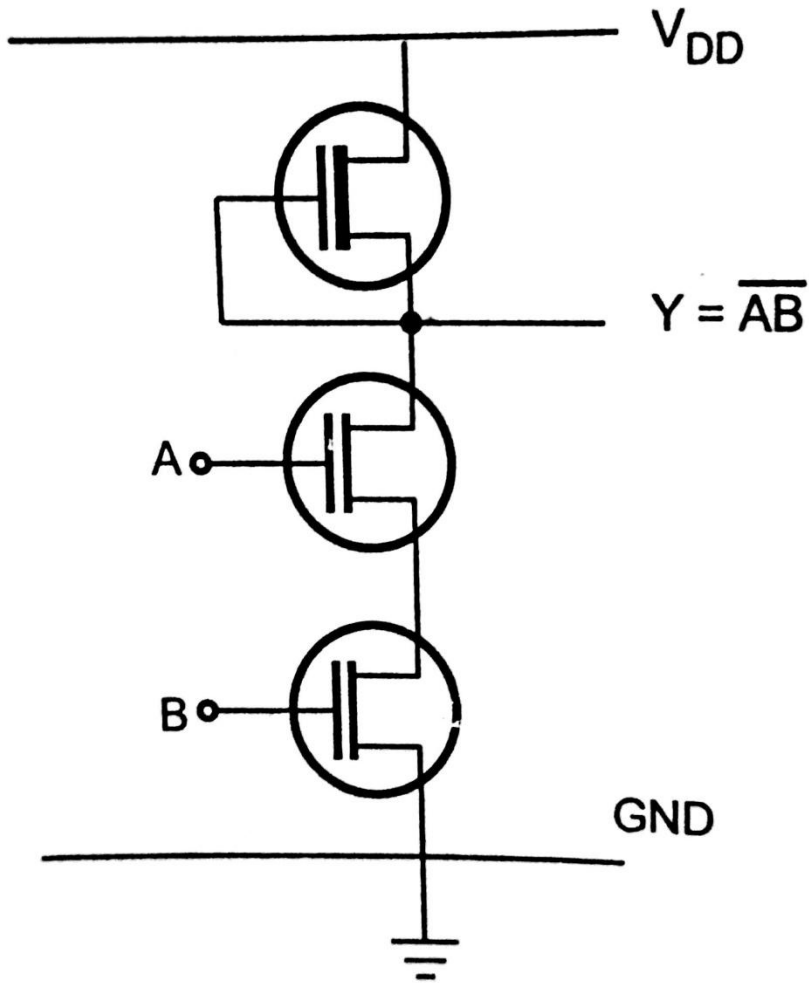

Three inputs nMOS NOR Gate

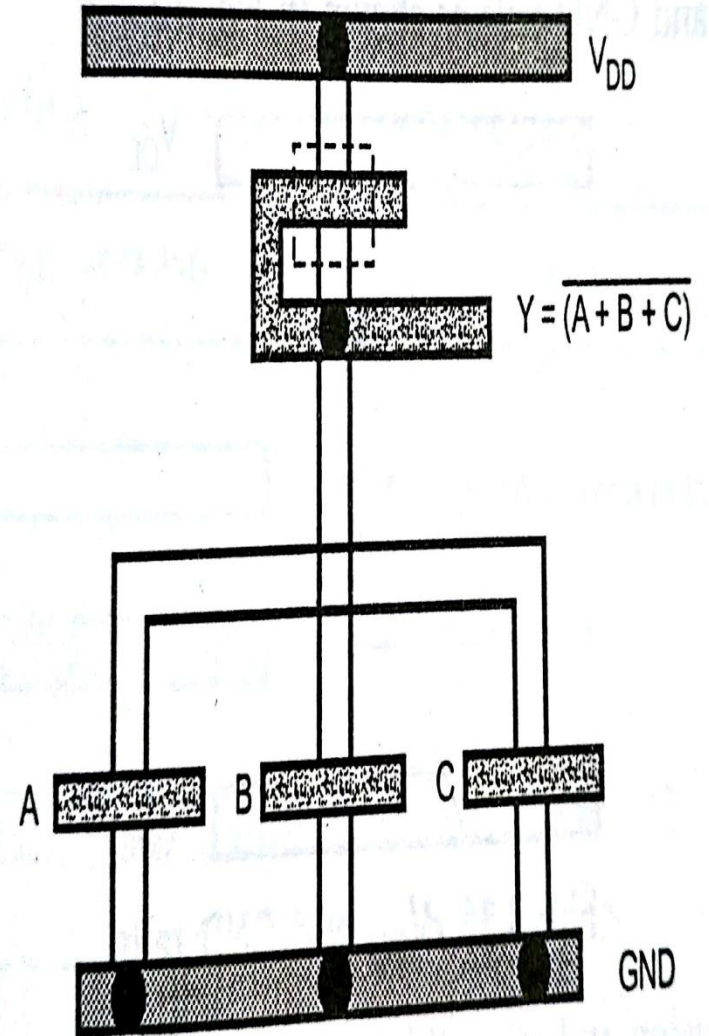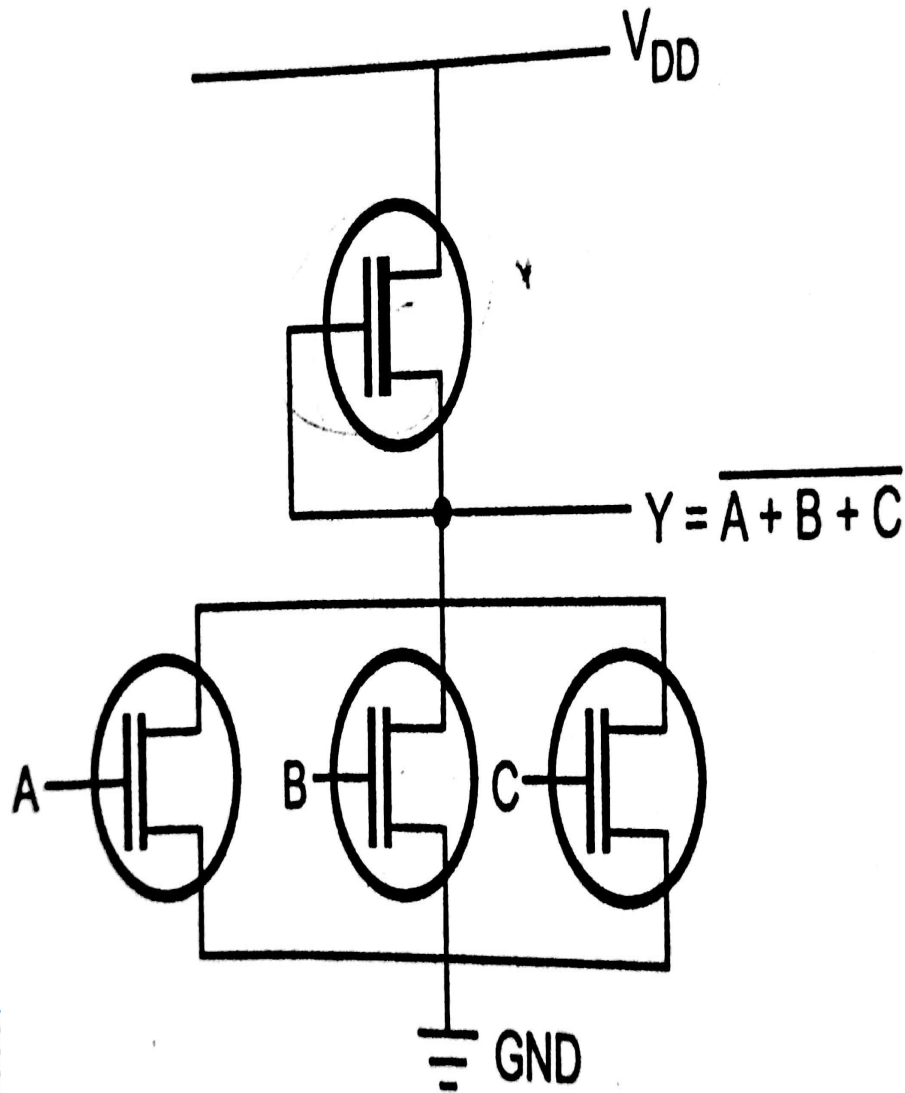

Transmission Gate(TG)

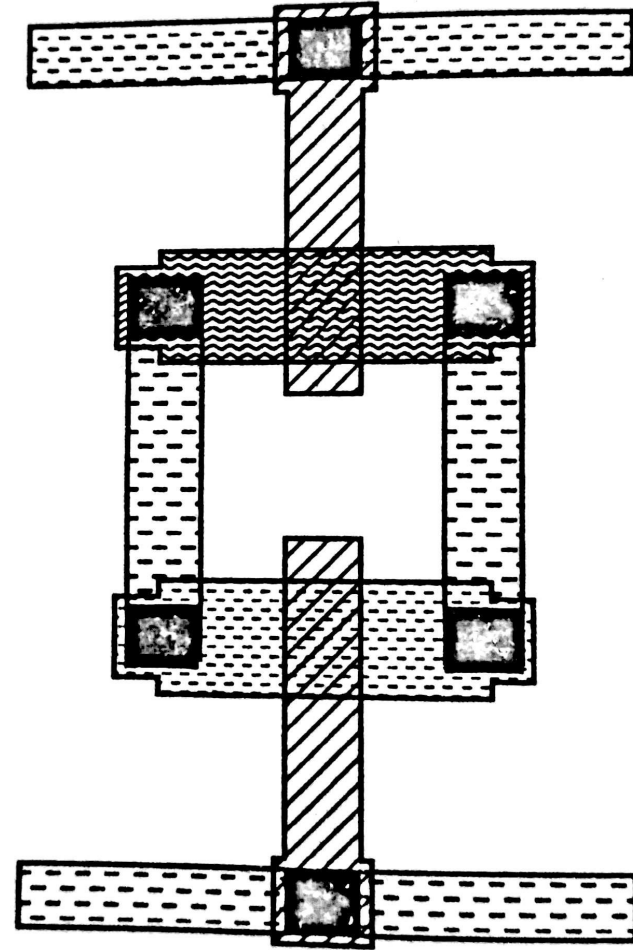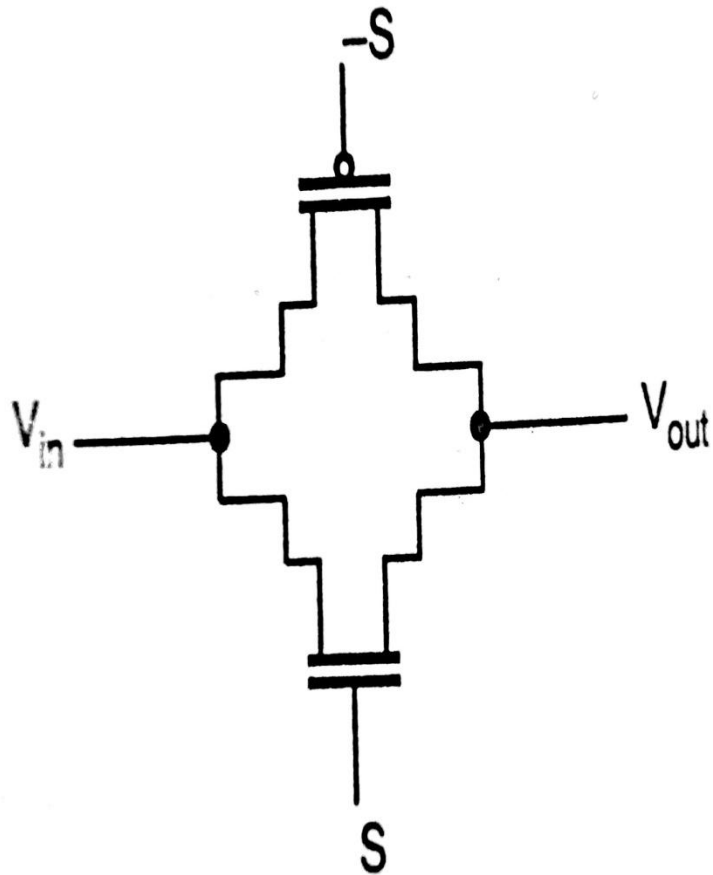

Before the cell can be constructed from a transistor schematic it is necessary to develop a strategy for the cell's basic layout. Stick Diagrams are a means for the design engineer to visualize the cell routing and transistor placement.

Method: Stick diagrams are constructed in two steps.


1) The first step is to construct a logic graph of the schematic (Figure1).

A) Identify each transistor by a unique name of its gate signal (A, B, C, D, E in the example of Figure1).

B) Identify each connection to the transistor by a unique name (1,2,3,4 in the example of Figure 1).

Fig 1: Schematic and Graph

$$F = (AB) + E + (CD)$$

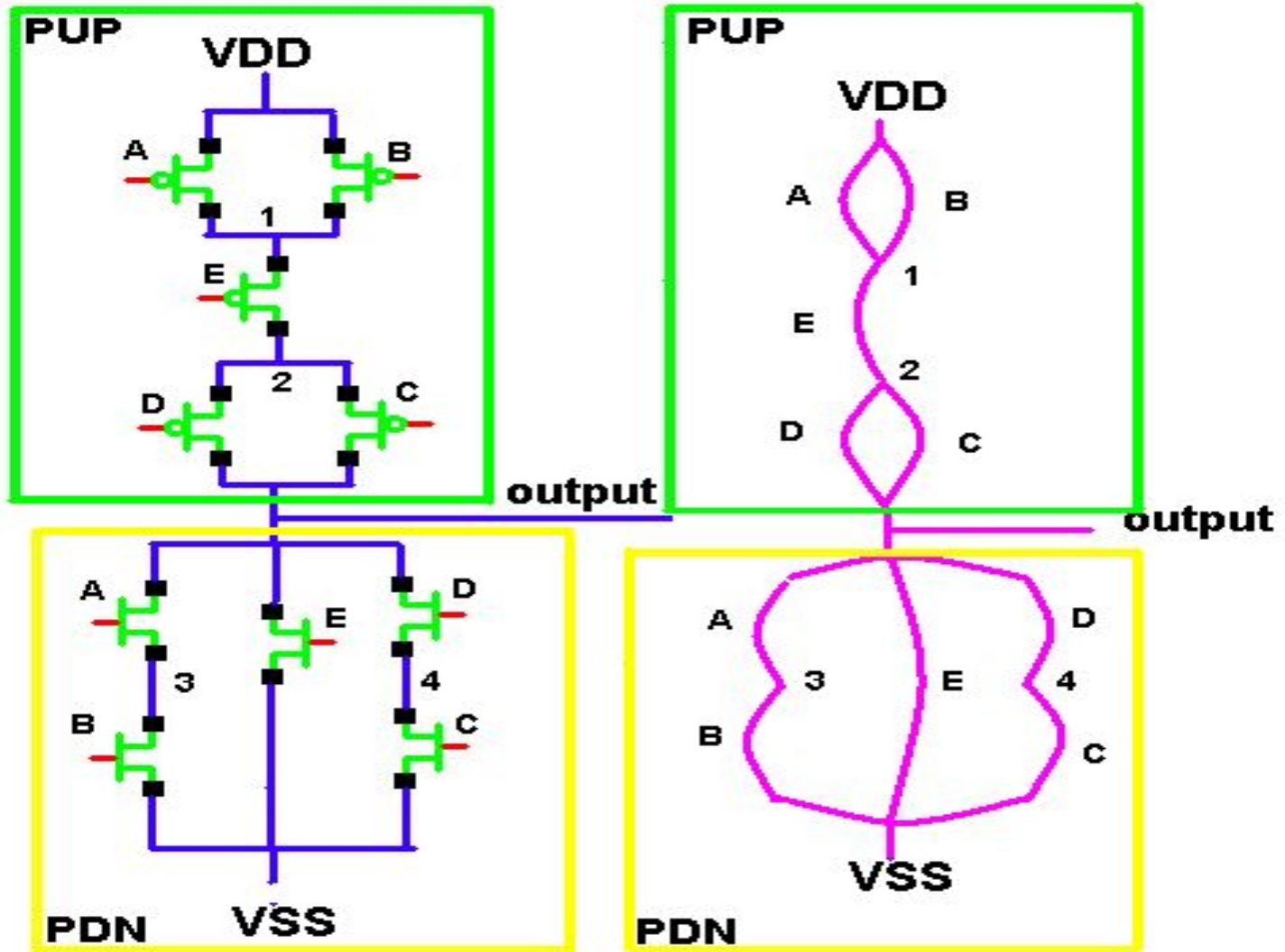

2) The second step is to construct one Euler path for both the Pull up and Pull down network (Figure 2).

A) Euler paths are defined by a path that traverses each node in the path, such that each edge is visited only once.

B) The path is defined by the order of each transistor name.

i) If the path traverses transistor A then B then C. Then the path name is {A, B, C}

C) The Euler path of the Pull up network must be the same as the path of the Pull down network.


D) Euler paths are not necessarily unique.

F) It may be necessary to redefine the function to find a Euler path.

$$\mathbf{i) F = E + (CD) + (AB) = (AB) + E + (CD)}$$

Fig 2: Euler Path

$$F = (AB)+E+(CD)$$

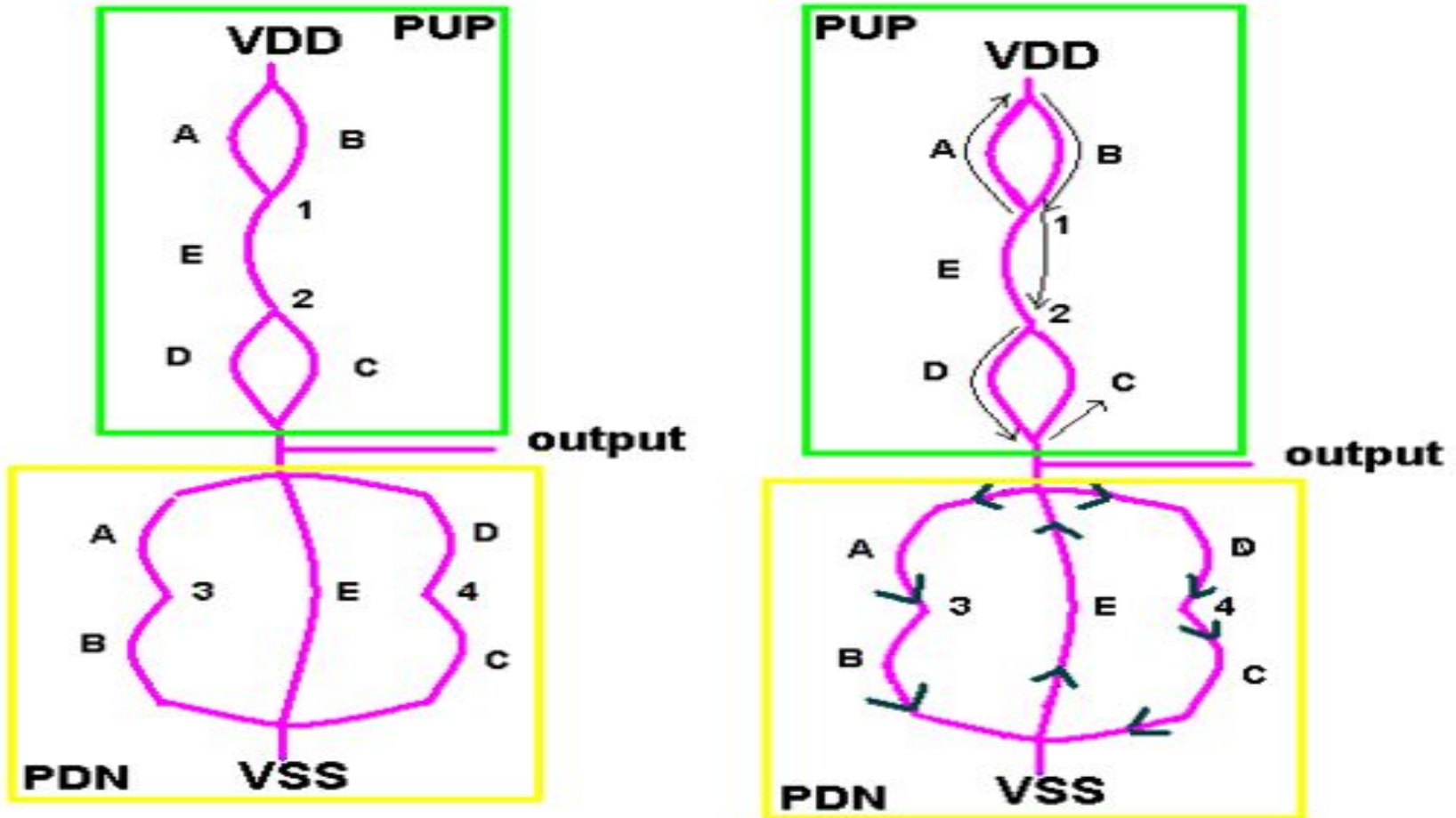

EULER PATH = {A,B,E,D,C}


Connection label layout

- A)** Trace two green lines horizontally to represent the NMOS and PMOS devices.
- B)** Trace the number of inputs (5 in this example) vertically across each green strip. These represent the gate contacts to the devices that are made of Poly.
- C)** Surround the NMOS device in a yellow box to represent the surrounding Pwell material.
- D)** Surround the PMOS device in a green box to represent the surrounding Nwell material.
- E)** Trace a blue line horizontally, above and below the PMOS and NMOS lines to represent the Metal 1 of VDD and VSS.
- F)** Label each Poly line with the Euler path label, in order from left to right.
- G)** Place the connection labels upon the NMOS and PMOS devices.

Connection label layout

EULER PATH = {A,B,E,D,C}

— METAL 1
— POLY
— ACTIVE

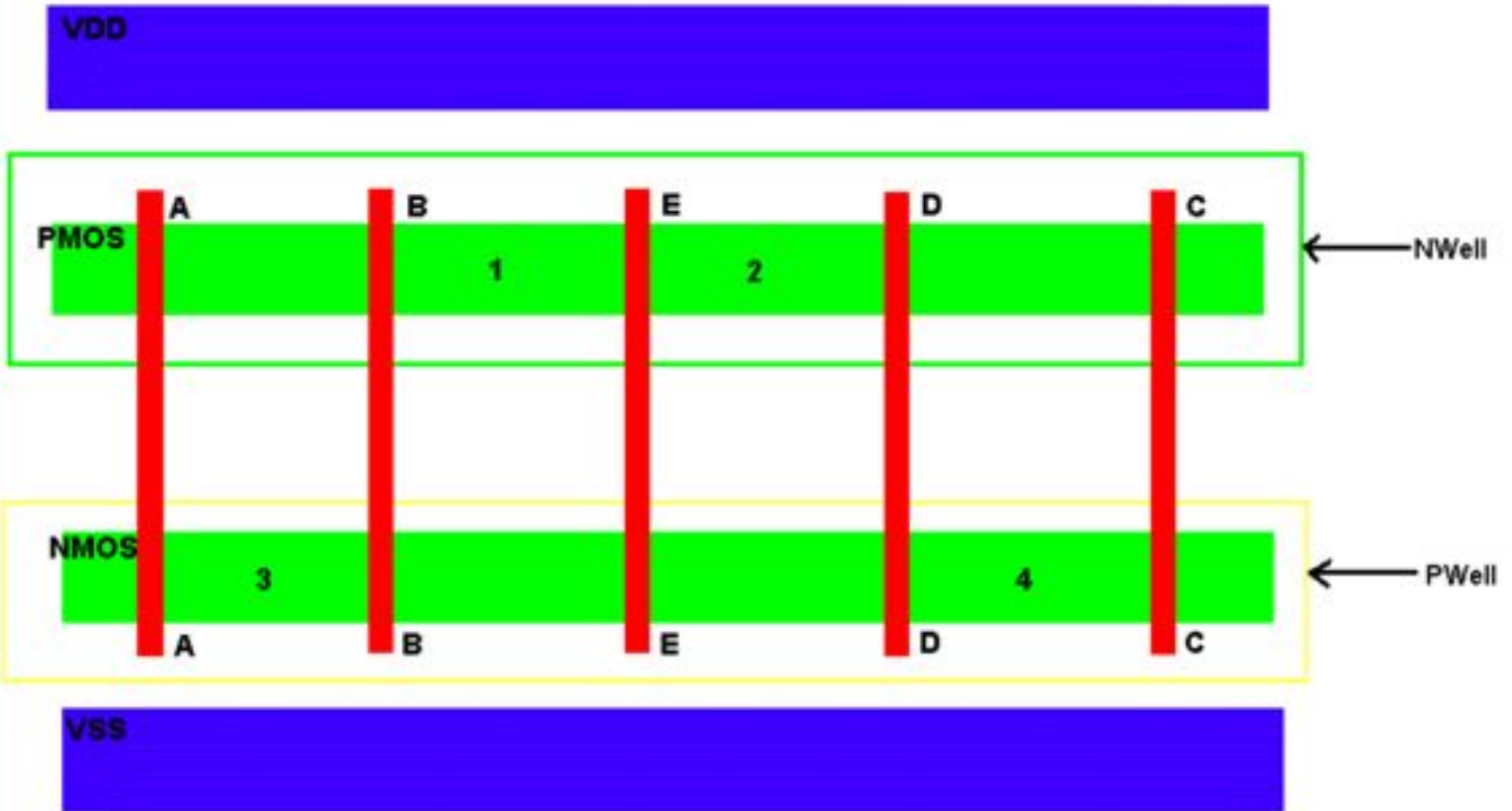

Interconnection of the Device

- A)** Notice that Poly and Metal 1 can overlap.
- B)** Avoid routing signals that are side by side for long lengths. This adds capacitance to the device.
- C)** Avoid all interconnect overlap if possible. This adds capacitance to the device.
- D)** Strive for simplicity. This will later provide the smallest and fastest devices.
- E)** You can use Poly, Metal 2, and even Active to interconnect your device.
 - i)** Poly and especially Active adds resistance to you device.
 - ii)** Avoid using Metal 2 if possible. Metal 2 is another layer to your device that you will probably need in the next hierarchy up.

Stick Diagram, Interconnected

